

Chapters 25: Circuit theory



Tuesday October 4th

****Mini Exam 3 on Thursday****


- DC circuits
 - Kirchoff's 2nd law (loop law)
 - Energy transfer in DC circuits
 - Internal resistance of a battery
 - Kirchoff's 1st law (node law)
- Examples
 - Network circuit with 1 battery
 - Parallel batteries
 - Complex circuit
- Thursday will involve capacitors

Reading: up to page 426 in the text book (Ch. 25)

DC Circuits

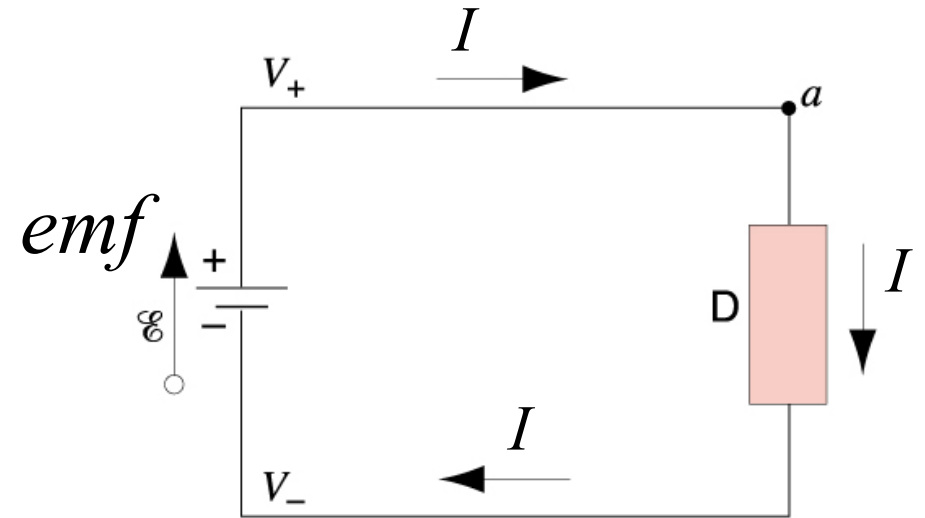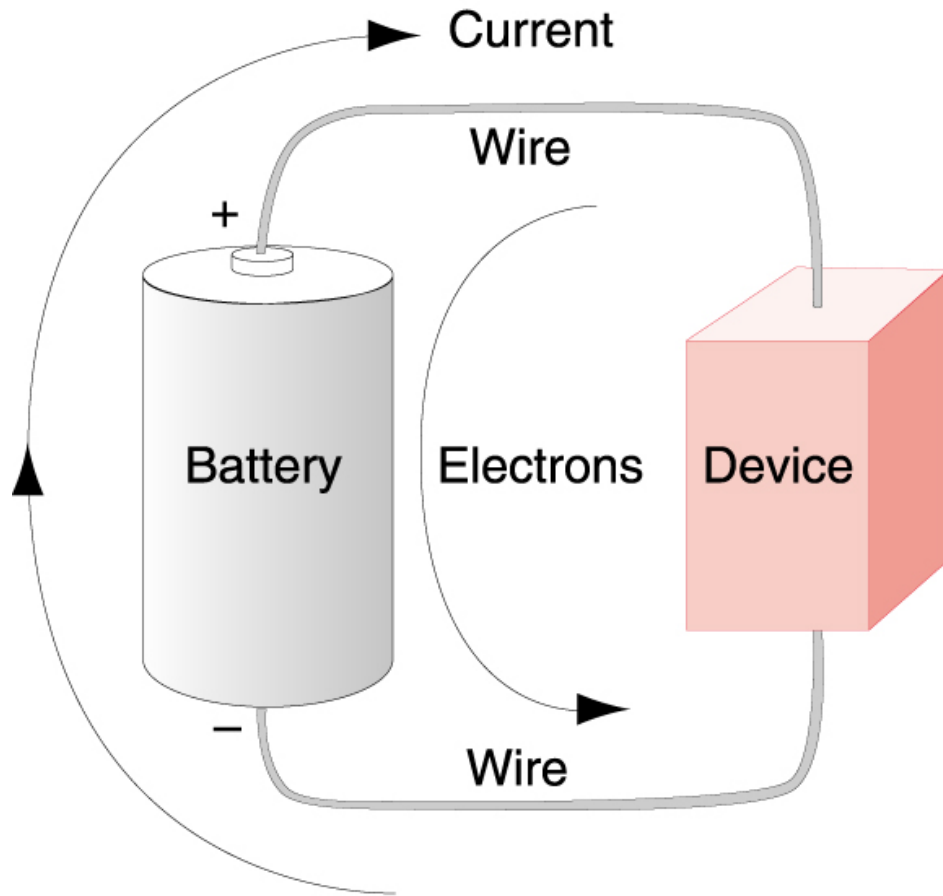

EMF = electromotive force

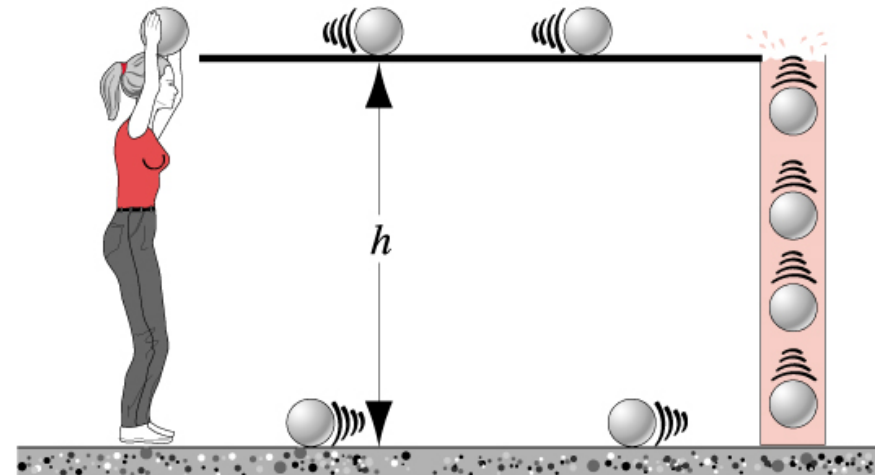


Electromotive force (emf)

- Source of electrical energy in a circuit.


$$\varepsilon = dW / dQ \quad \text{SI unit: joule/Coulomb}$$

- Represents the potential energy provided to each coulomb of charge that passes through the device.
- IT IS NOT A FORCE!!!
- Most often, emf is provided by a battery (a chemical cell).
- The emf is the same as the potential difference between the negative and positive terminals of a battery WHEN NO CURRENT FLOWS.
- In general, when a current flows, the potential difference at the terminals of a battery is lower than the emf.
- An emf can also store energy.

Circuit analysis - series circuits

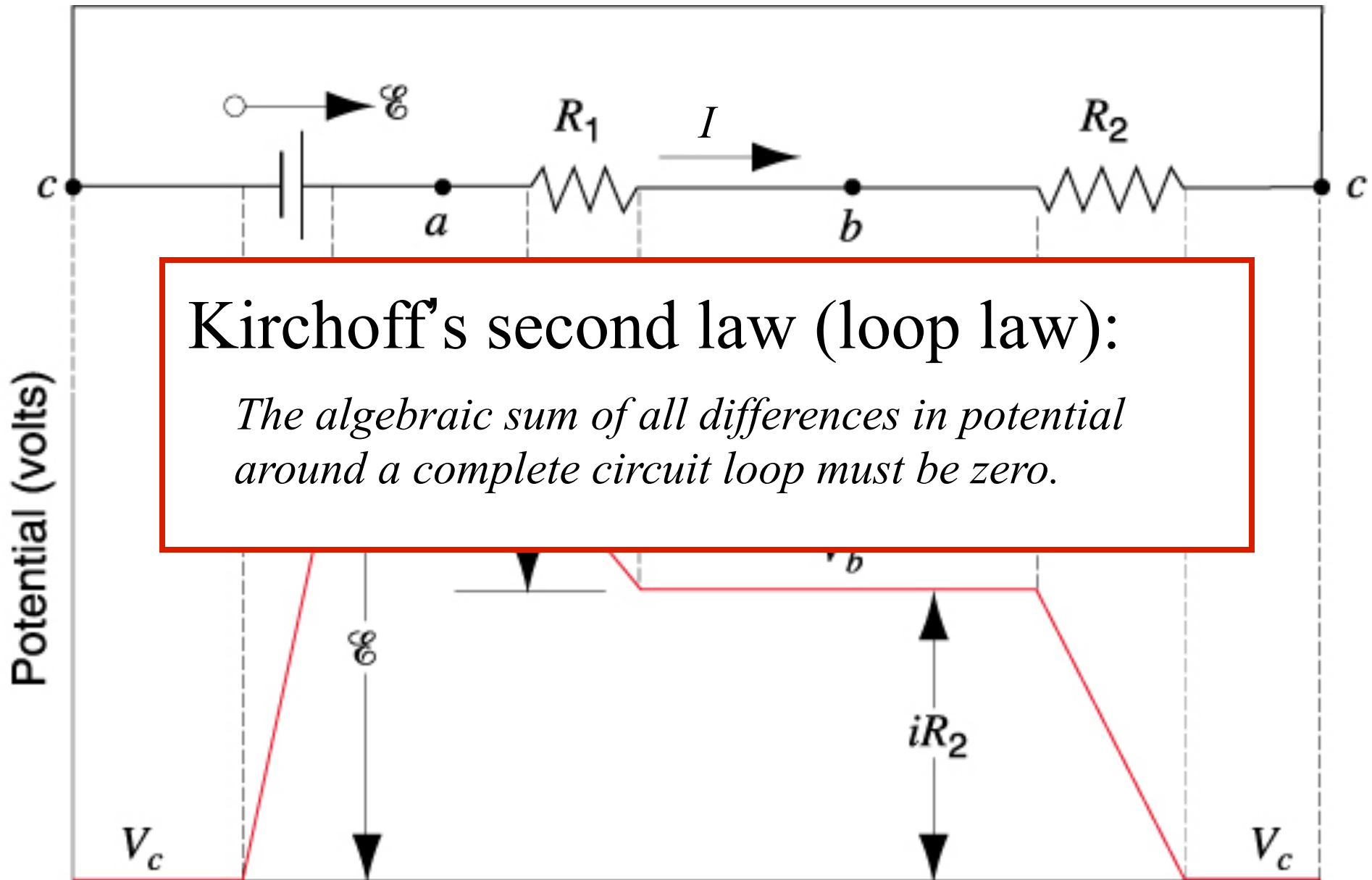

Circuit analysis - series circuits

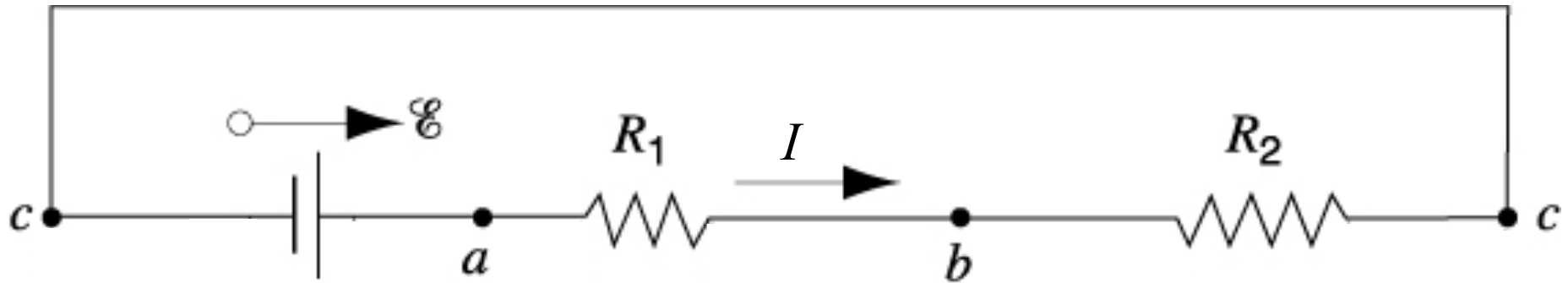

Kirchoff's second law:

The algebraic sum of all differences in potential around a complete circuit loop must be zero.

$$\Rightarrow \mathcal{E} - IR_1 - IR_2 = 0$$

$$\mathcal{E} = I(R_1 + R_2) = IR_{eq}$$

$$R_{eq} = R_1 + R_2, \text{ in general } R_{eq} = \sum_i R_i$$

Energy transfer in electric circuits

- A 1V battery does work by providing each coulomb of charge that leaves its positive terminal 1 joule of energy.
- If charge flows at a rate of 1 coulomb per second, then the battery does work at a rate of 1 joule per second, i.e.

$$\text{Power} = \frac{\text{joule}}{\text{coulomb}} \times \frac{\text{coulomb}}{\text{second}} = \frac{\text{joule}}{\text{second}} = \text{watt}$$

$$P = \varepsilon I = dW / dt$$

- In a resistor, energy is lost in an amount iR per coulomb.


$$\Rightarrow P_{\text{charge}} = I \times \Delta V = I(-IR) = -I^2 R$$

$$P_{\text{heat}} = I^2 R = (V / R)^2 R = V^2 / R$$


- This process is irreversible.

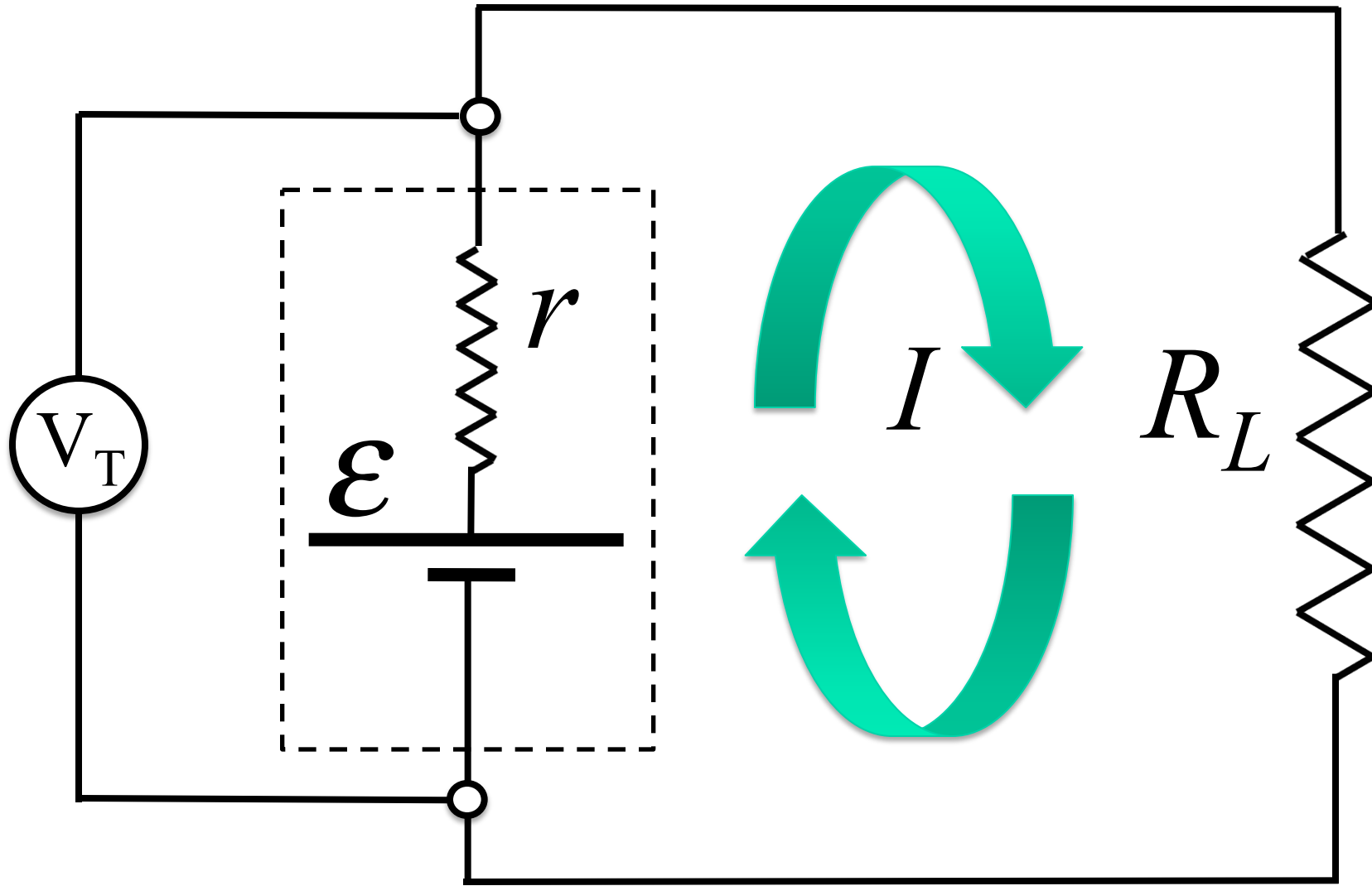Example: Battery with internal resistance

R_L = load resistance; r = internal resistance; \mathcal{E} = battery *e.m.f.*




Example: parallel resistances

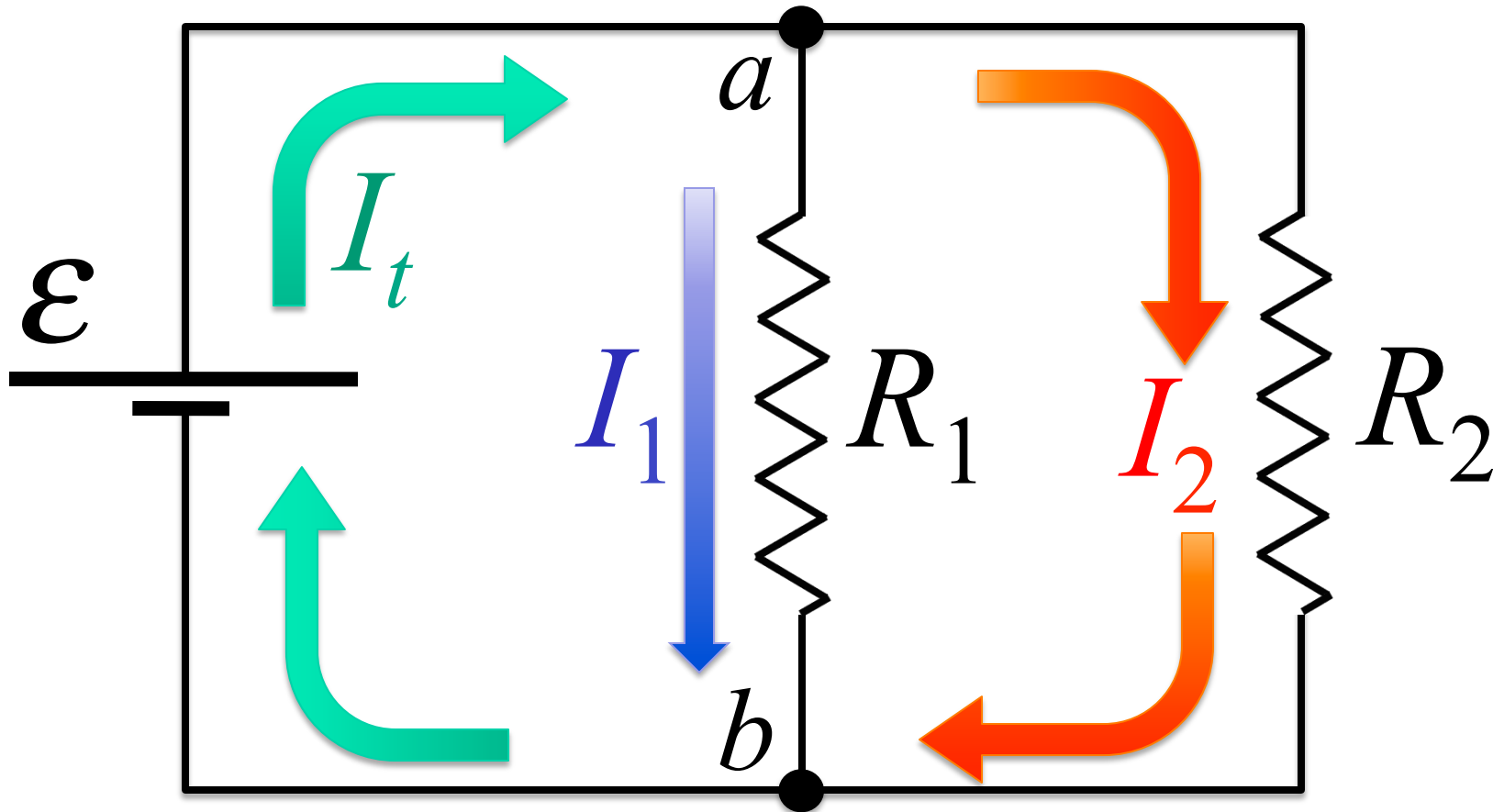

Kirchoff's first law (node law):


Algebraic sum of currents at any node is zero: $I_t - I_1 - I_2 = 0$

Example: parallel resistances

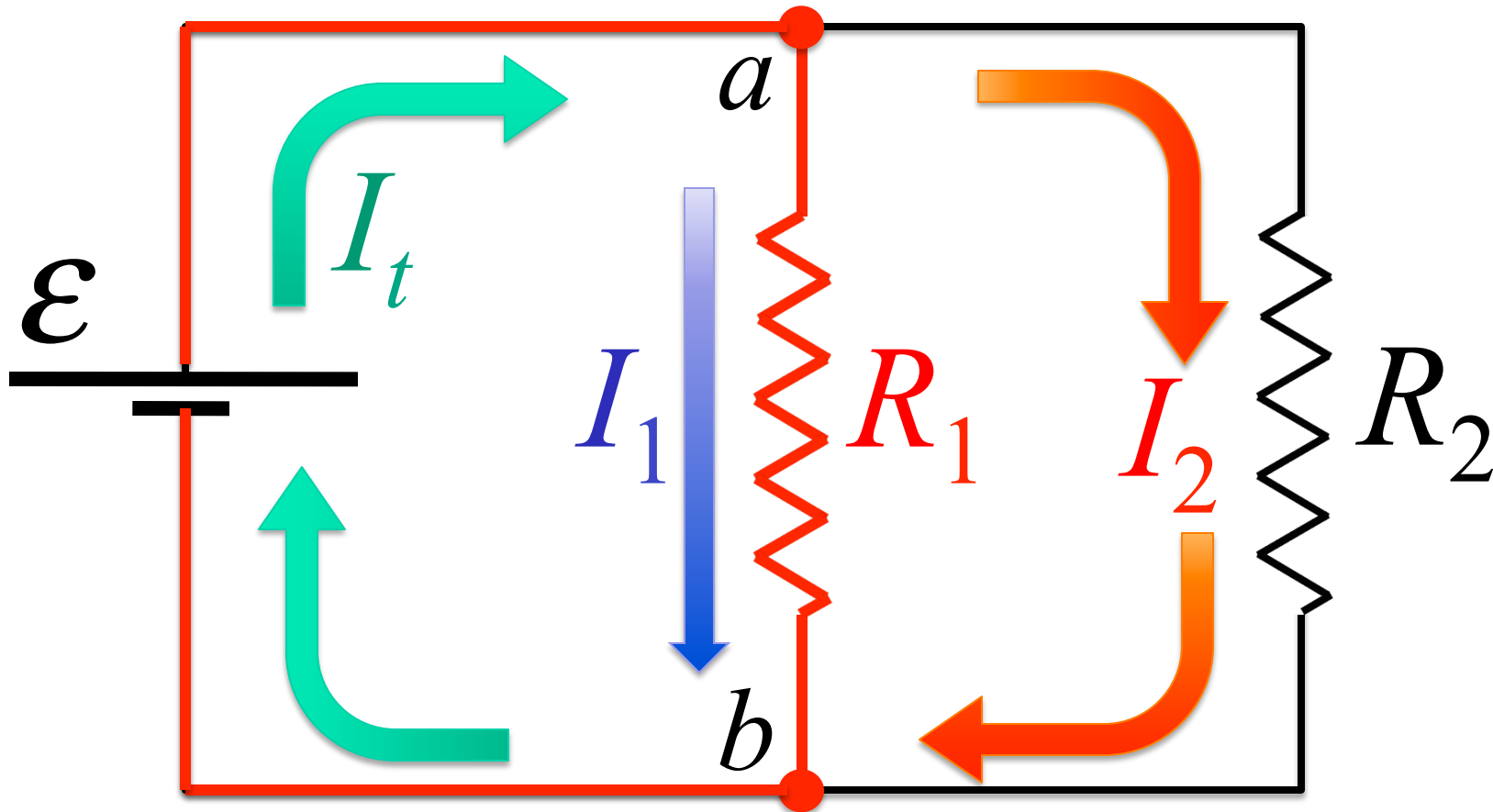


Loop 1

Example: parallel resistances

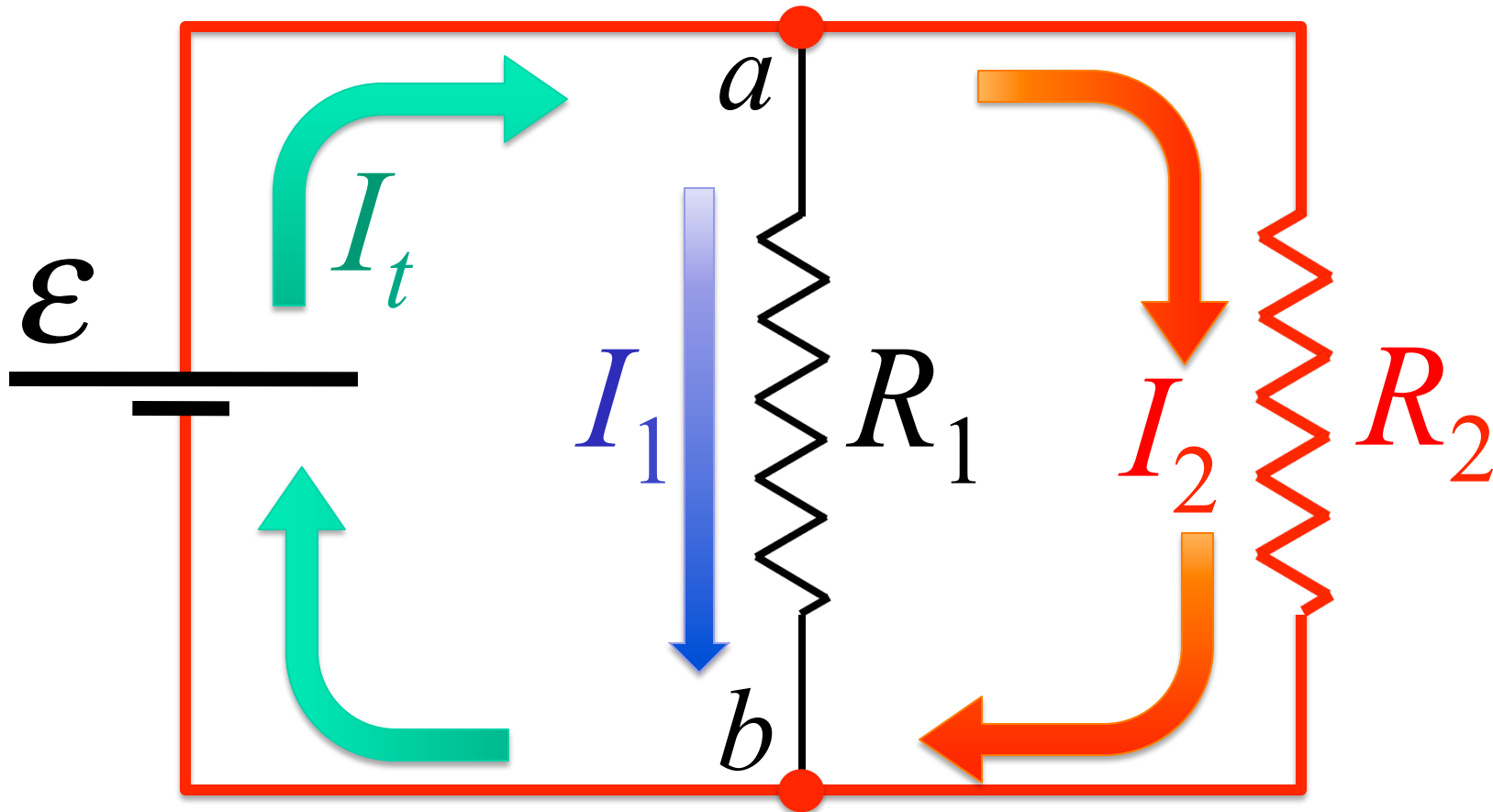


Loop 2

Example: parallel resistances

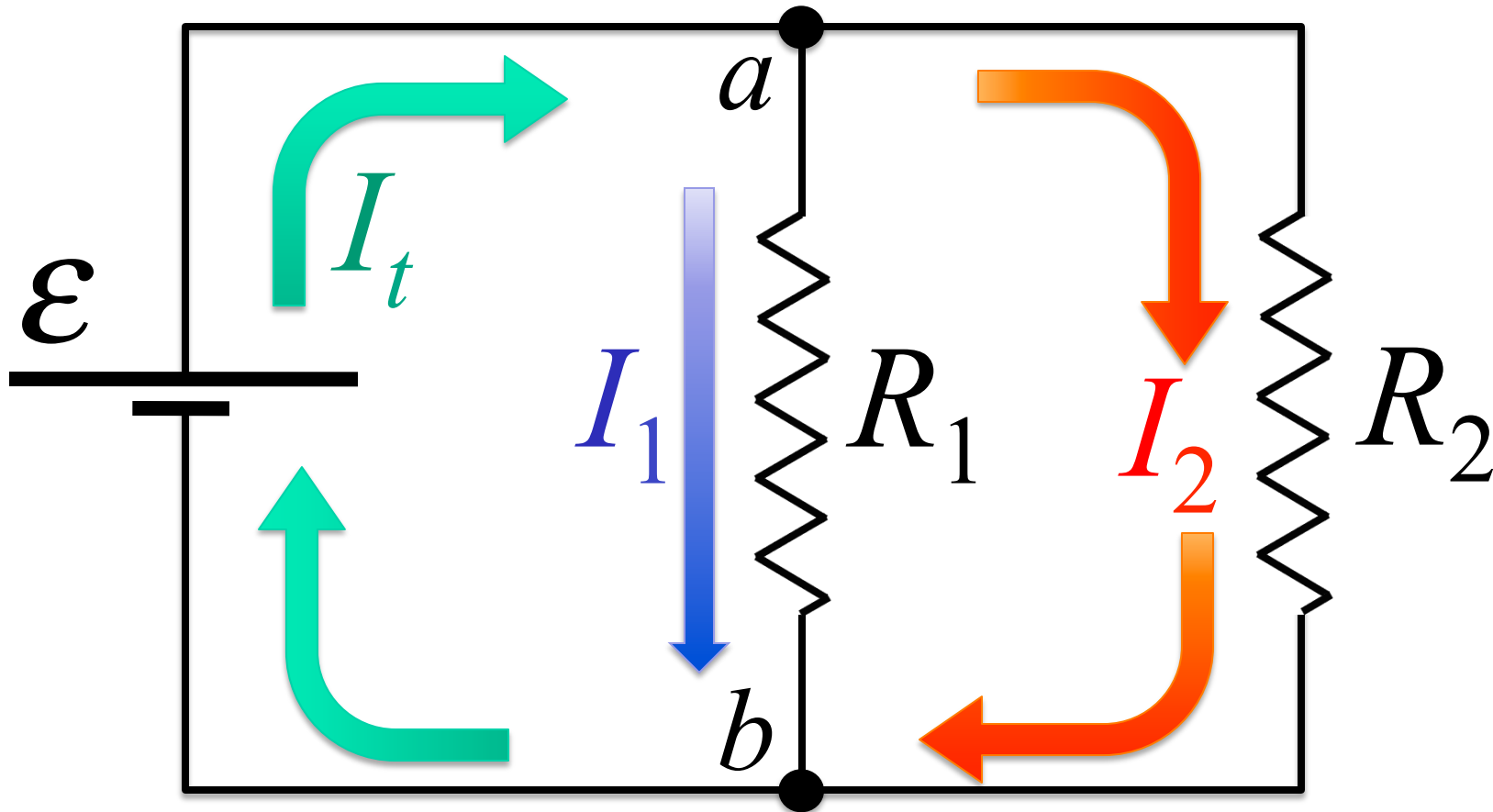

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}, \text{ in general } \frac{1}{R_{eq}} = \sum_i \frac{1}{R_i}$$


Example: parallel/series resistors

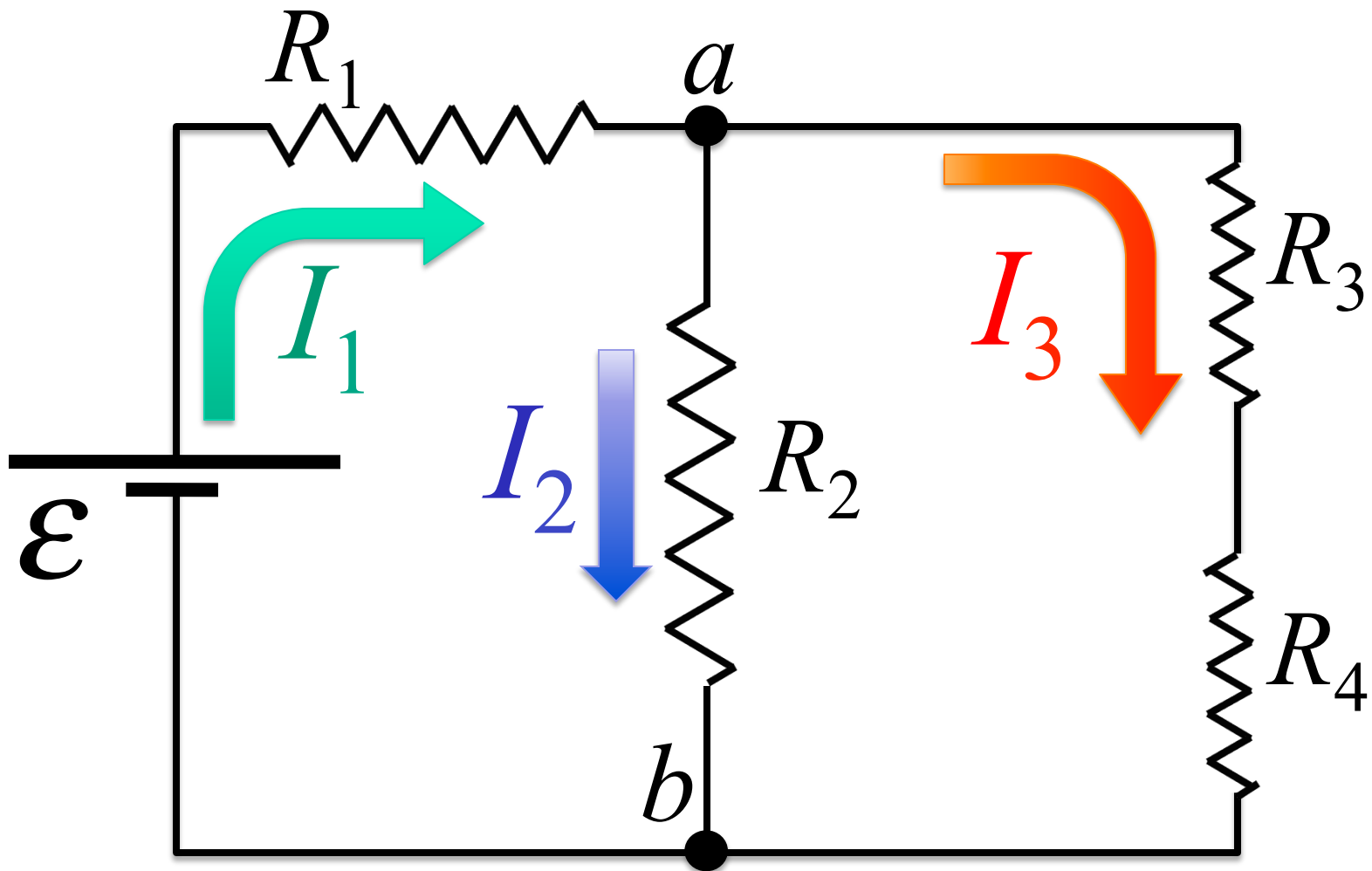

Deduce: (a) current through R_2 ; (b) power dissipation in R_4 ; and voltage across R_3 .

$$\mathcal{E} = 10 \text{ V}; R_1 = 5 \text{ } \Omega; R_2 = 16 \text{ } \Omega; R_3 = 7 \text{ } \Omega; R_4 = 12 \text{ } \Omega$$


Example: multiple batteries

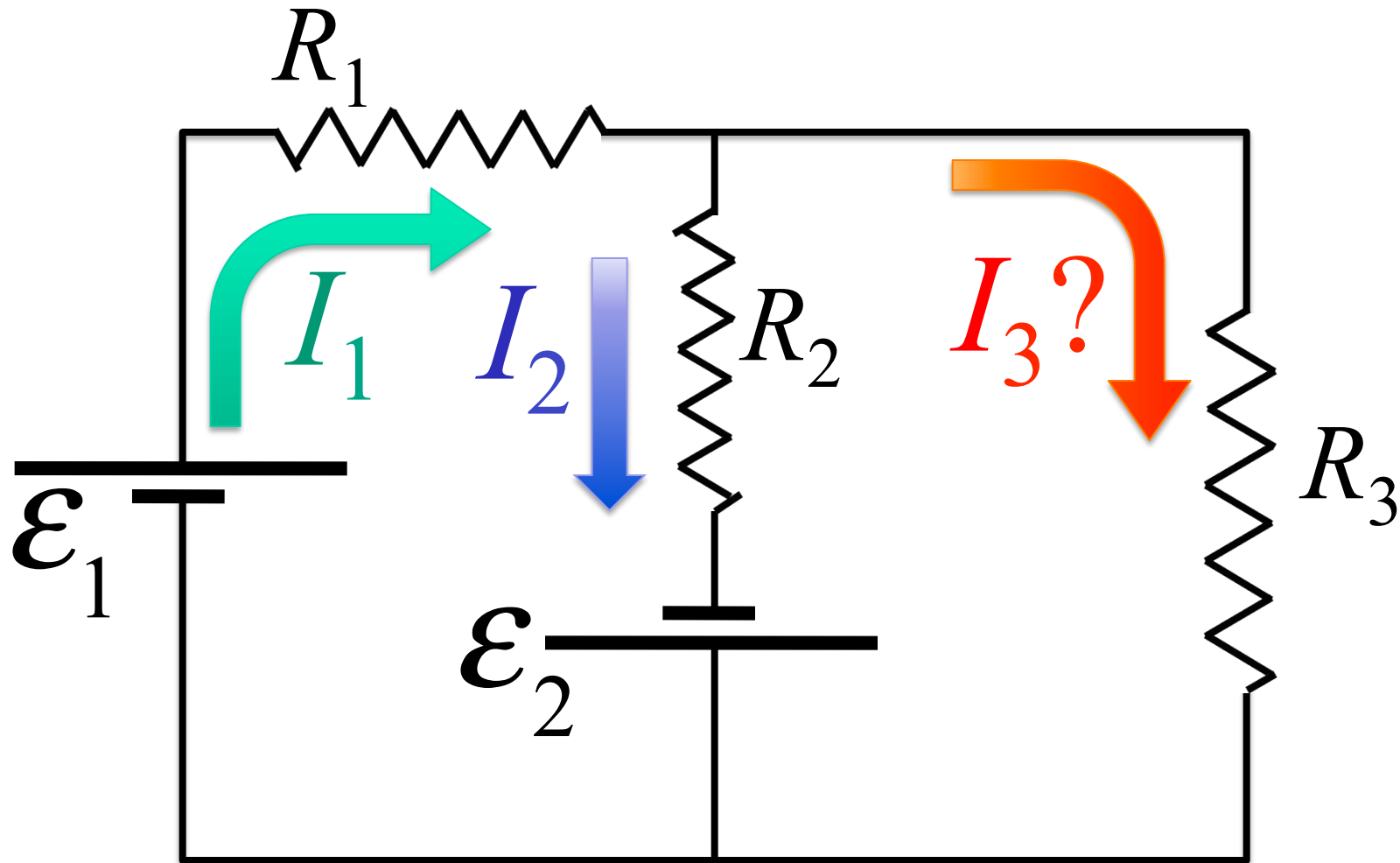

Find current I_3

$$\mathcal{E}_1 = 10 \text{ V}; \quad \mathcal{E}_2 = 20 \text{ V}; \quad R_1 = 15 \text{ } \Omega; \quad R_2 = 6 \text{ } \Omega; \quad R_3 = 7 \text{ } \Omega.$$


Example: multiple batteries

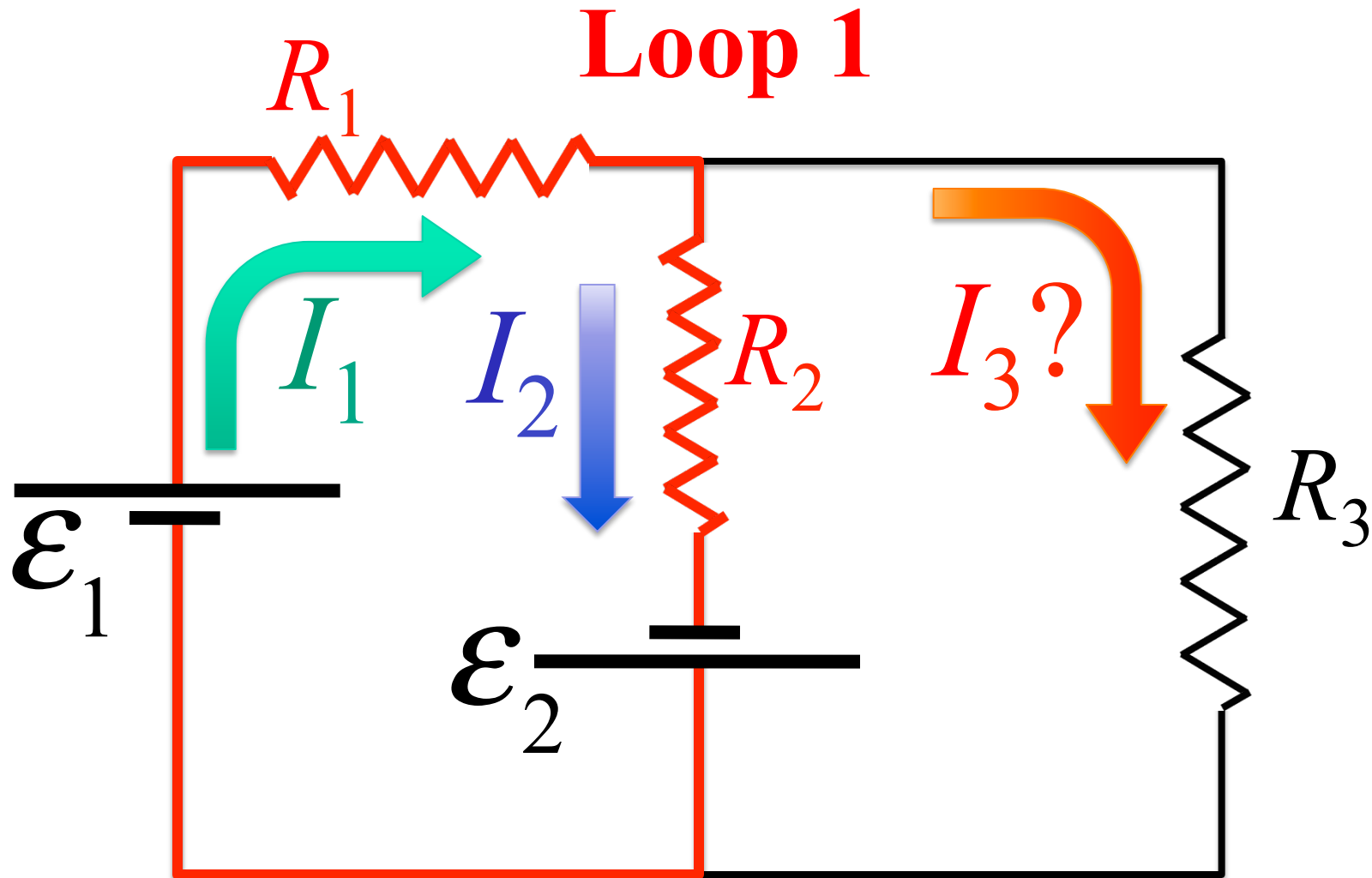

Find current I_3

$$\mathcal{E}_1 = 10 \text{ V}; \quad \mathcal{E}_2 = 20 \text{ V}; \quad R_1 = 15 \text{ } \Omega; \quad R_2 = 6 \text{ } \Omega; \quad R_3 = 7 \text{ } \Omega.$$

Example: multiple batteries

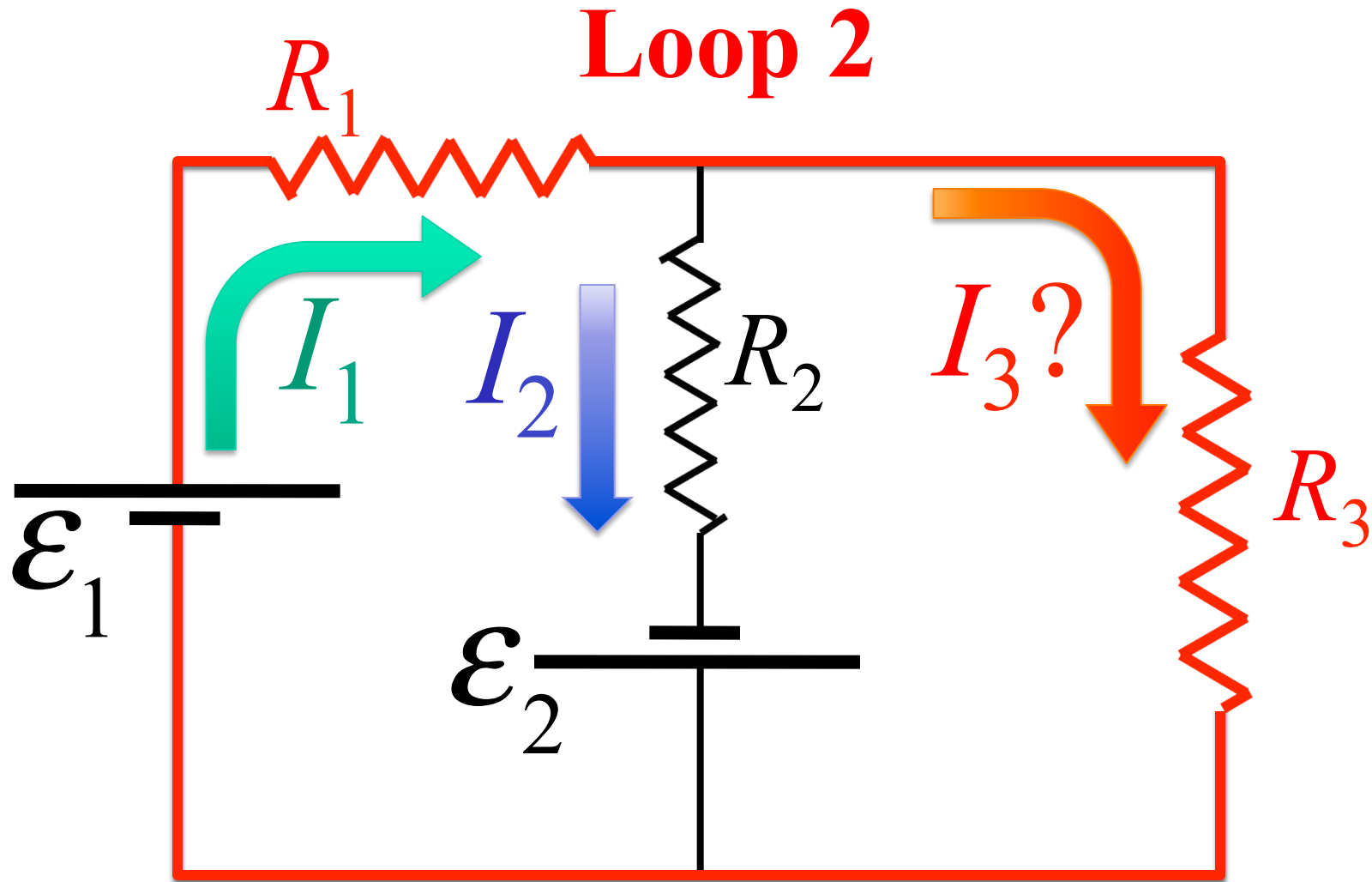


Find current I_3

$$\mathcal{E}_1 = 10 \text{ V}; \quad \mathcal{E}_2 = 20 \text{ V}; \quad R_1 = 15 \text{ } \Omega; \quad R_2 = 6 \text{ } \Omega; \quad R_3 = 7 \text{ } \Omega.$$

Example: multiple batteries

Loop 3

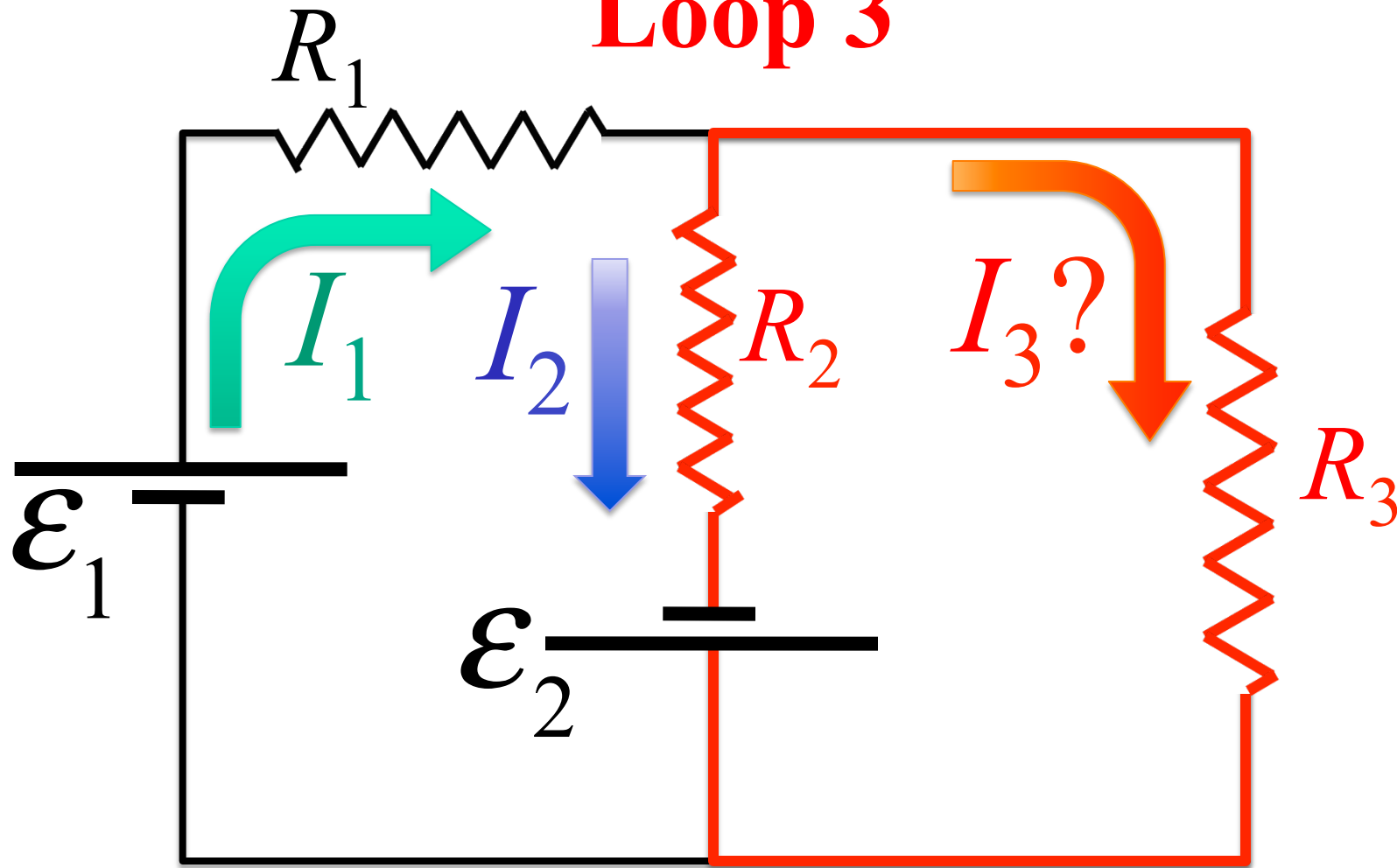

Find current I_3

$$\mathcal{E}_1 = 10 \text{ V}; \quad \mathcal{E}_2 = 20 \text{ V}; \quad R_1 = 15 \text{ } \Omega; \quad R_2 = 6 \text{ } \Omega; \quad R_3 = 7 \text{ } \Omega.$$